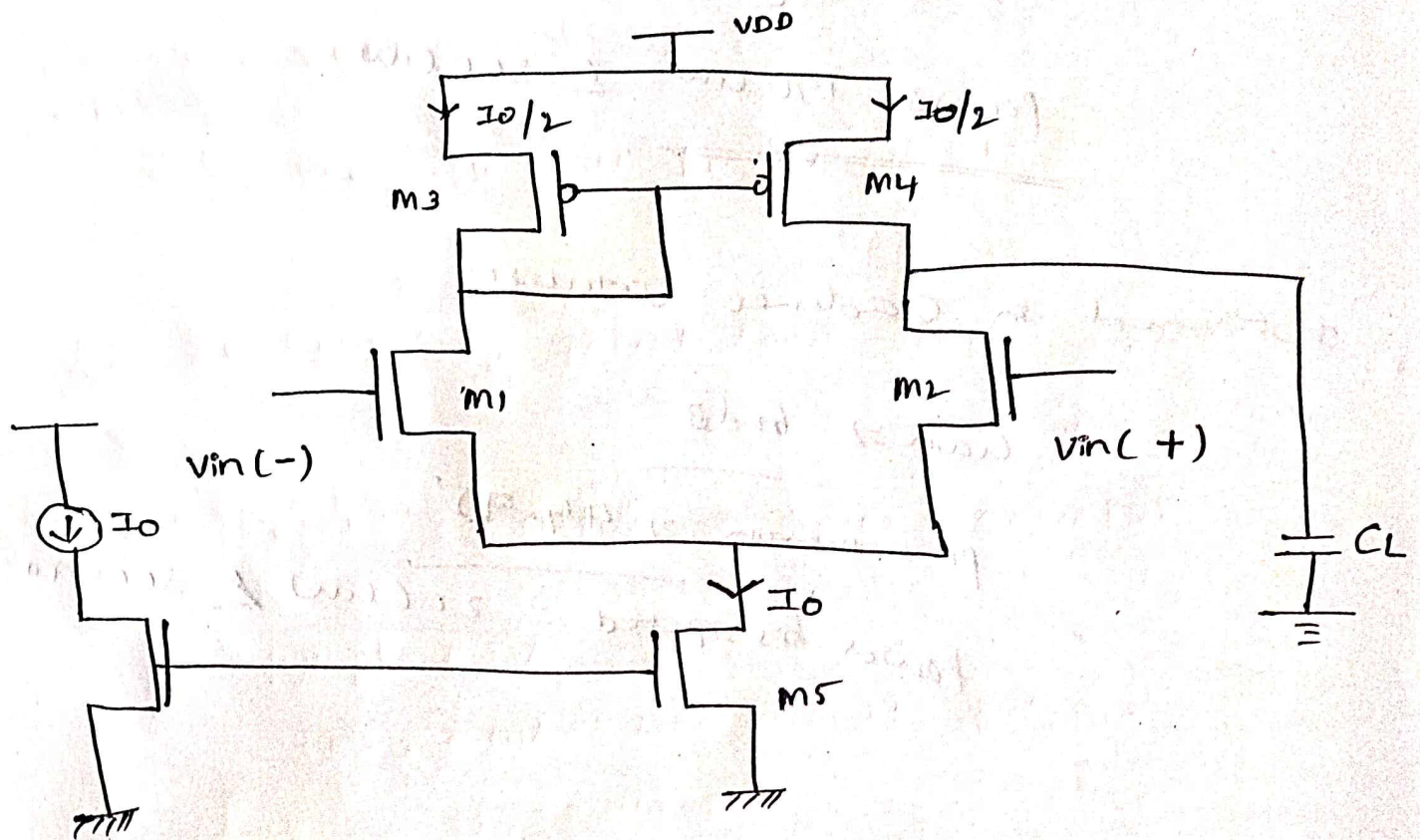


Differential Amplifier



* specifications *

$$V_{DD} = 1.8V$$

$$A_{DC} = 100 \Rightarrow 20 \log_{10} 100 \Rightarrow 40dB$$

$$C_L = 10pF$$

$$SR = 5V/\mu sec$$

$$GBW \approx 5MHz$$

$$\left. \begin{aligned} I_{CMR(+)} &= 1.6V \\ I_{CMR(-)} &= 0.8V \end{aligned} \right\}$$

such that mosfets doesnot go into Triode region

from slew rate, $SR = dv/dt$

we know that $Q = CV$

$$I = \frac{dQ}{dt} = C \frac{dv}{dt}$$

$$\frac{I}{C} = \frac{dv}{dt}$$

for output $\frac{I_O}{C_L} = \frac{dv}{dt} = \text{slew rate.}$

$$I_O = C_L \left(\frac{dv}{dt} \right)$$

$$I_O = (10 \times 10^{-12}) \left(\frac{5V}{\mu\text{sec}} \right)$$

$$\underline{I_O \Rightarrow 50 \mu\text{A}}$$

Let us take a part of circuit

for M_1 to be in saturation

$$V_{DS} > V_{GS} - V_{t1}$$


$$V_D > V_G - V_{t1}$$

$$V_X > 1.6 - 0.45$$

$$V_X > 1.15$$

Let

$$\underline{V_X = 1.2}$$

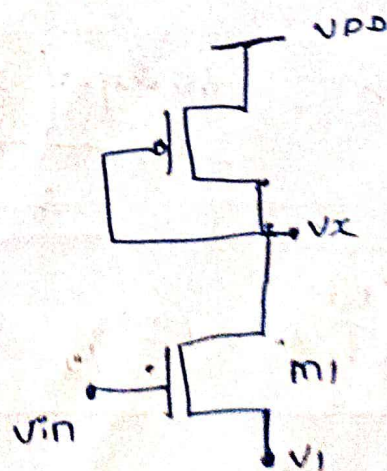

$$V_{DS3} = V_{DD} - V_X$$

$$V_{DS3} = 1.8 - 1.2$$

$$V_{DS3} = 0.6V$$

$$\text{As } I_0 = 50 \mu A$$

I_3 and I_4 will be $25 \mu A$ each.

Do DC operating point and find μ_{nCOX} & μ_{pCOX} parameters

$$\text{Let } \mu_{nCOX} = 300 \mu A/V^2 \quad \& \quad \mu_{pCOX} = 60 \mu A/V^2$$

$$|V_{thp}| = 0.5V$$


$$V_{thn} = 0.4V \quad \text{from circuit's analysis.}$$

$$I_3 = \mu_{pCOX} \left(\frac{W}{L} \right) \frac{(V_{GG} - |V_{thp}|)^2}{2}$$


$$25 \mu A = \frac{60 \mu A/V^2 \left(\frac{W}{L} \right)}{2} [0.6 - 0.5]^2$$

$$\boxed{\left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_4 = 84}$$

from small signal parameters of mosfet,

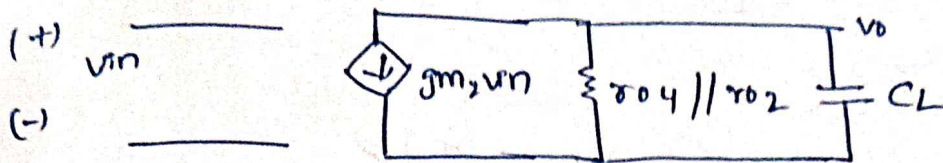

$$\frac{v_o}{r_{o4} || r_{o2}} + \frac{v_o}{\left(\frac{1}{sC_L}\right)} - g_{m2} v_{in} = 0$$

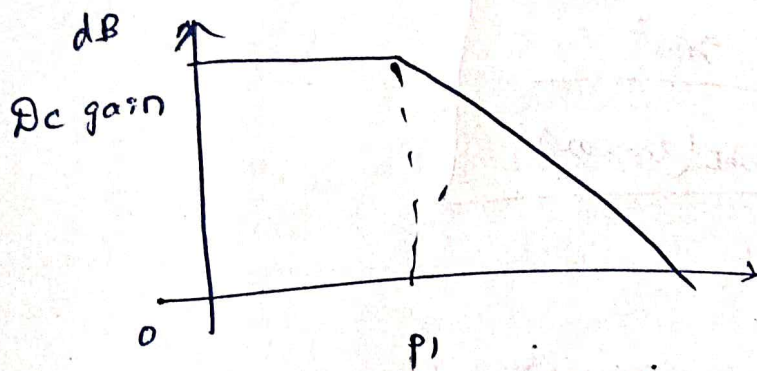

$$\frac{v_o}{v_{in}} \Rightarrow \frac{-g_m (r_{o2} || r_{o4})}{1 + sC_L (r_{o2} || r_{o4})} \Rightarrow \frac{\text{DC gain}}{\left(1 + \frac{s}{p_1}\right)}$$

$$\text{DC gain} \Rightarrow g_m (r_{o2} || r_{o4})$$

$$GBW = \text{DC gain} (p_1)$$

$$GBW = \frac{g_{m1}}{sC_L} \rightarrow 2\pi C_L$$

$$g_{m1} \approx 5 \text{ MHz} (2\pi \times 10 \text{ pF})$$

$$g_{m1} = 3/4 \text{ u}$$

$$I_D = \mu n C_{ox} \left(\frac{W}{L} \right) \frac{(V_{GS} - V_{th})^2}{2}$$

$$\frac{\partial I_D}{\partial V_{GS}} = g_m = \mu n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{th})$$

$$g_m^2 \Rightarrow 2 I_D \mu n C_{ox} \frac{W}{L}$$

$$\ast \left(\frac{W}{L} \right) = \frac{g_m^2}{2 I_D (\mu n C_{ox})}$$

$$\left(\frac{W}{L} \right)_{1,2} \Rightarrow \frac{(314 \mu)^2}{2(25 \mu)(300 \mu)} \Rightarrow 7$$

$$\left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_2 = 7$$

for MS

$$V_{in_{min}} > V_{gs1} + V_{dsat5}$$

$$I_D = \frac{\mu_{n102} \left(\frac{W}{L} \right)}{2} (V_{gs1} - V_{th})^2$$

250A ←

$$V_{gs1} = 0.6V$$

$$V_{dsat} \leq 0.2$$

$$To \text{ get } \left(\frac{W}{L} \right)_5$$

$$I_D \Rightarrow \frac{\mu_{n102} \left(\frac{W}{L} \right)}{2} (V_{gs1} - V_{th})^2$$

500A

$$\left(\frac{W}{L} \right)_5 = 9$$

After simulation

Gain is around $\approx 35.7dB$.

$f_{BW} = 4.8MHz$.